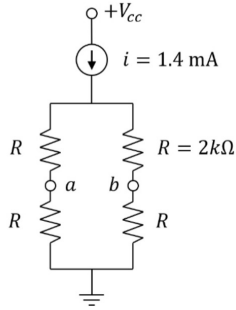



Pre-Lab Questions

For each of the four circuits shown below compute the voltages v_a , v_b , v_{cm} , and v_{dm} , where v_{cm} and v_{dm} is the common mode voltage and differential mode voltage between v_a and v_b , respectively.


1.)



2.)

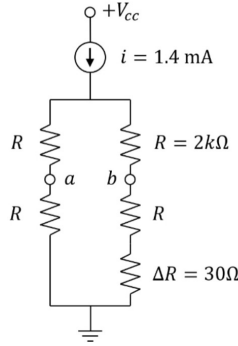

1)

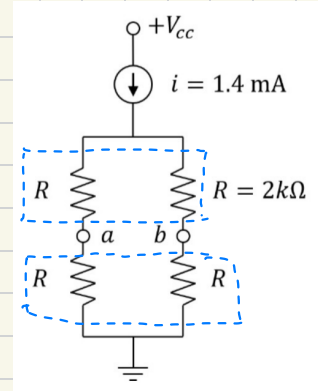

$$i = \frac{V_a}{R} \Rightarrow \frac{V_a}{R \parallel R}$$

$$V_a = i (R \parallel R)$$

$$V_a = 1.4 \text{ mA} (2 \text{ k}\Omega \parallel 2 \text{ k}\Omega)$$

$$V_a = 1.4 \text{ mA} (1 \text{ k}\Omega)$$

$$V_a = 1.4 \text{ V}$$


$$a = b$$

$$\underline{V_a = 1.4 \text{ V}} \quad \underline{V_b = 1.4 \text{ V}}$$

$$V_{cm} = \frac{V_1 + V_2}{2} = \frac{V_a + V_b}{2} = \frac{1.4 \text{ V} + 1.4 \text{ V}}{2} = \frac{2.8 \text{ V}}{2} = \underline{1.4 \text{ V}} \quad V_{cm} = \underline{1.4 \text{ V}}$$

$$V_{dm} = \frac{V_1 - V_2}{2} = \frac{V_a - V_b}{2} = \frac{1.4 \text{ V} - 1.4 \text{ V}}{2} = \frac{0}{2} = \underline{0 \text{ V}} \quad V_{dm} = \underline{0 \text{ V}}$$

2)

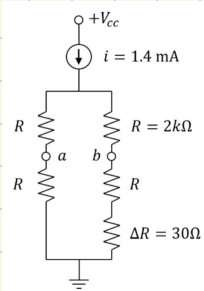

$$V_a = i (R \parallel R)$$

$$= 1.4 \text{ mA} (2 \text{ k}\Omega \parallel 2 \text{ k}\Omega)$$

$$= 1.4 \text{ mA} (1 \text{ k}\Omega)$$

$$\underline{V_a = 1.4 \text{ V}}$$

$$V_b \neq V_a \quad V_b > V_a$$

$$V_b = i (R \parallel R + \Delta R)$$

$$V_b = 1.4 \text{ mA} (2 \text{ k}\Omega \parallel 2 \text{ k}\Omega + 30 \Omega)$$

$$V_b = 1.4 \text{ mA} \left(\frac{(2 \text{ k}\Omega)(2 \text{ k}\Omega)}{2 \text{ k}\Omega + 2 \text{ k}\Omega} + 30 \Omega \right)$$

$$V_b = 1.4109 \text{ V} \approx \underline{1.41 \text{ V}}$$


$$\rightarrow \left(\frac{1}{R} + \frac{1}{2 \text{ k}\Omega} \right)^{-1} \rightarrow \frac{R \cdot 2 \text{ k}\Omega}{R + (2 \text{ k}\Omega)}$$

$$\underline{V_b = 1.41 \text{ V}}$$


$$V_{cm} = \frac{V_1 + V_2}{2} = \frac{V_a + V_b}{2} = \frac{1.4V + 1.41V}{2} = \frac{2.81}{2} = 1.405V \quad \underline{V_{cm} = 1.405V}$$

$$V_{dm} = \frac{V_1 - V_2}{2} = \frac{V_a - V_b}{2} = \frac{1.4V - 1.41V}{2} = \frac{-0.01}{2} = -0.005V \quad \underline{V_{dm} = -5mV}$$


3.)

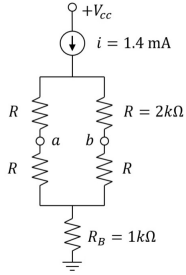

4.)

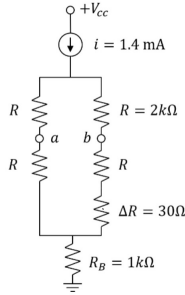

3.)

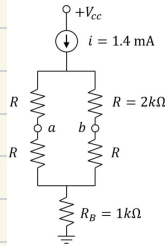

$$\begin{aligned} V_a &= IR \\ &= 1.4mA [2k\Omega || 2k\Omega] \\ &= 1.4mA [1k\Omega] \end{aligned}$$

$$\underline{V_a = 1.4V}$$


$$\begin{aligned} V_b &= IR \\ &= 1.4mA [2k\Omega || 2k\Omega + 1k\Omega] \\ &= 1.4mA [2k\Omega || 3k\Omega] \\ &= 1.4mA \left[\frac{3,000\Omega \cdot 2,000\Omega}{5,000\Omega} \right] \\ &= 1.4mA [1.2k\Omega] \end{aligned}$$

$$\underline{V_b = 1.68V}$$

$$V_{cm} = \frac{V_1 + V_2}{2} = \frac{V_a + V_b}{2} = \frac{1.4V + 1.68V}{2} = \frac{3.08V}{2} = 1.54V \quad \underline{V_{cm} = 1.54V}$$

$$V_{dm} = \frac{V_1 - V_2}{2} = \frac{V_a - V_b}{2} = \frac{1.4V - 1.68V}{2} = \frac{-0.28V}{2} = -0.14V \quad \underline{V_{dm} = -0.14V}$$

4)

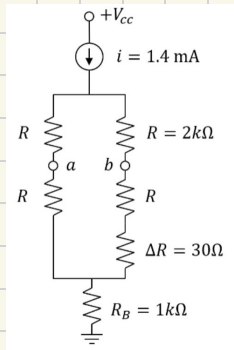

$$\begin{aligned}
 V_a &= 1.4 \text{ mA} (2 \text{ k}\Omega \parallel 2 \text{ k}\Omega) \\
 &= 1.4 \text{ mA} (1 \text{ k}\Omega) \\
 &= \underline{1.4 \text{ V}}
 \end{aligned}$$

$$\underline{V_a = 1.4 \text{ V}}$$

$$\begin{aligned}
 V_b &= 1.4 \text{ mA} (2 \text{ k}\Omega \parallel 2030 \Omega) \\
 &= 1.4 \text{ mA} \left(\frac{2,000 \cdot 2030}{2000 + 2030} \right) \\
 &= \underline{1.41 \text{ V}}
 \end{aligned}$$

$$\frac{1.41 \text{ V}}{1 \text{ k}\Omega} = i \text{ [from } R_B] \quad i = 1.41 \text{ mA}$$

$$V_D = 1.41 \text{ mA} (1 \text{ k}\Omega) + 1.41 \text{ V} = \underline{2.82 \text{ V}} \rightarrow \underline{V_D = 2.82 \text{ V}}$$

$$V_{cm} = \frac{1.4 \text{ V} + 2.82 \text{ V}}{2} = \frac{4.22 \text{ V}}{2} = \underline{2.11 \text{ V}}$$

$$V_{dm} = \frac{1.4 \text{ V} - 2.82 \text{ V}}{2} = \frac{-1.42}{2} = \underline{-0.71 \text{ V}}$$