

Pre-Lab Questions

1. The BJT in Figure 1 is in a forward-active region with $V_{BE} = 0.7V$, $I_B = 12mA$, and $V_{CE} = 2.5V$.

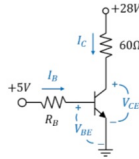


Figure 1: BJT in Common Emitter Configuration

- What is the power dissipated in the BJT?
 - What is the power dissipated in the load?
 - What is the power efficiency of the circuit?
2. The BJT in Figure 1 is in a saturation region with $V_{BE} = 0.8V$, $I_B = 30mA$, and $V_{CE} = 0.3V$.

- What is the power dissipated in the BJT?
- What is the power dissipated in the load?
- What is the power efficiency of the circuit?

a)

$$P = V \cdot I$$

$$= (2.5V) (425mA)$$

$$= 1.0625W$$


$$\boxed{P = 1.06W}$$

b)

$$P = I^2 \cdot R$$

$$= (0.425)^2 \cdot (60) = \boxed{10.8375W}$$

1)

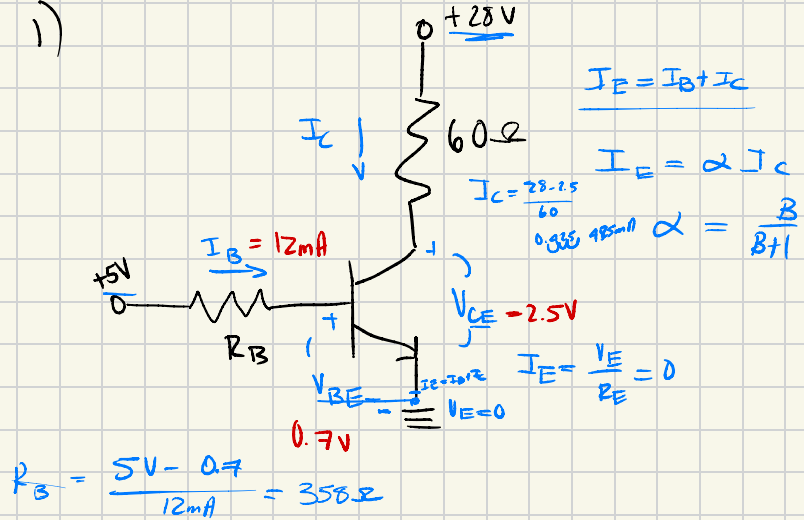

c)

$$\% = \frac{10.8375W}{10.8375W + 1.06W} \times 100\%$$

$$= \boxed{91.09\%}$$

2. The BJT in Figure 1 is in a saturation region with $V_{BE} = 0.8V$, $I_B = 30mA$, and $V_{CE} = 0.3V$.

- What is the power dissipated in the BJT?
- What is the power dissipated in the load?
- What is the power efficiency of the circuit?

a) $P = V \cdot I$

$$= (0.3V)(461mA) = 0.1383$$
$$\boxed{P = 138.3 \text{ mW}}$$

b) $P = I^2 \cdot R$

$$= (0.461)^2 \cdot (60\Omega) = 12.75W$$
$$\boxed{P = 12.75W}$$

c) $\% = \frac{12.75W}{12.75W + 0.1383W} \times 100\%$

$$= \boxed{98.92 \%}$$

