

AS Rivas hux 960

Pre-Lab Questions

1. Compute the transfer function $H(j\omega)$ for the following non-inverting op-amp circuit.

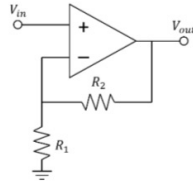


Figure 1: Non-inverting Op-Amp Circuit Diagram

Transfer function

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)}$$

- $Z_{R1} = R_1$
- $Z_{R2} = R_2$

$$V_{in} = Z_{R1}$$

$$V_{out} = Z_{R1} + Z_{R2}$$

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{Z_{R1} + Z_{R2}}{Z_{R1}} = \frac{R_1 + R_2}{R_1} \Rightarrow \boxed{1 + \frac{R_2}{R_1}}$$

2. Create the following circuit in PSpice, perform a time-domain simulation and provide a copy of the schematic and the graphed results in your prelab 4 submission.


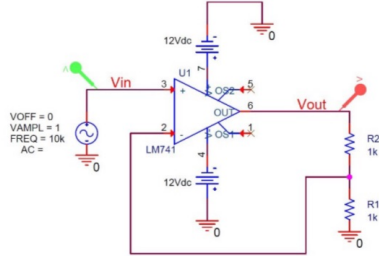
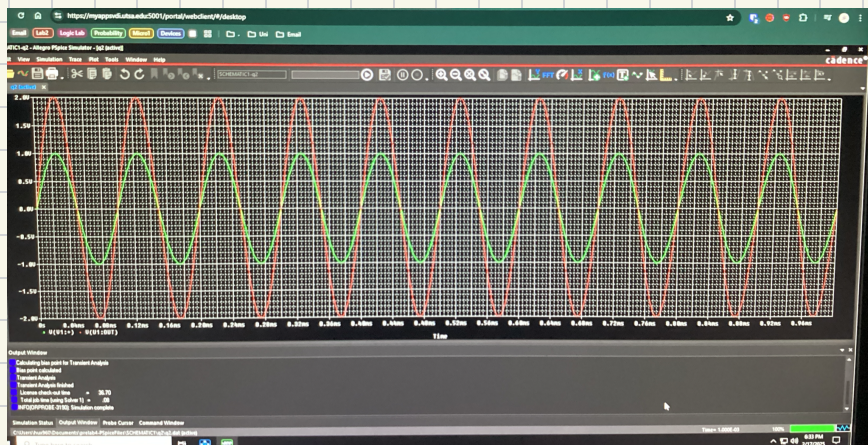


Figure 2: Non-inverting Op-amp Schematic with Voltage Probes

Note that:

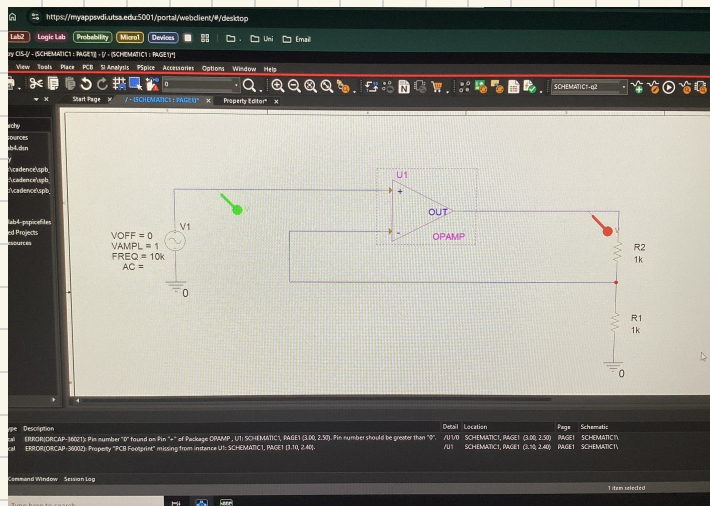- No connects need to be placed on pins 1 and 5 of the op-amp.
- Voltage sources need to be oriented such that negative voltage is supplied to pin 4 and positive voltage is supplied to pin 7.
- Under *Simulation Profile Settings* use 1ms for the 'Run To Time' setting, and use 1us for the 'Maximum Step Size' setting.



3. Modify the circuit from the previous prelab question by changing the voltage source parameters as well as the simulation profile setting and perform a frequency-domain simulation. Provide a copy of the schematic and the graphed results in your prelab 4 submission.

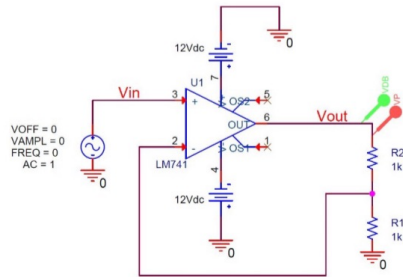


Figure 3: Non-inverting Op-amp Schematic with Gain and Phase Probes

- Make sure to change the simulation profile setting to AC Sweep/Noise and use 1 as the 'Start Frequency' parameter, use "100mega" as the 'End Frequency' parameter, and use 10 as the 'Points/Decade' parameter.
- Use the 'dB Magnitude of Voltage' and 'Phase of Voltage' probes from the **PSpice** > **Markers** > **Advanced** list.

[Provide the Pre-Lab answers separate from the lab report, and show your work.]

