

MATHEMATICS & SIGNALS

Complex Number Conversions:

- Rectangular to Polar: $r = \sqrt{x^2 + y^2}$, $\theta = \tan^{-1} \left(\frac{y}{x} \right)$
- Polar to Rectangular: $x = r \cos(\theta)$, $y = r \sin(\theta)$

System Impedances ($s = j\omega$):

- Resistor: $Z_R = R$
- Capacitor: $Z_C = \frac{1}{sC} = \frac{1}{j\omega C} = -j \frac{1}{\omega C}$
- Inductor: $Z_L = sL = j\omega L$

RMS Values (Standard Sinusoids):

- $V_{RMS} = \frac{V_{peak}}{\sqrt{2}}$
- $I_{RMS} = \frac{I_{peak}}{\sqrt{2}}$

CALCULUS RULES

Derivatives:

$$\frac{d}{dt}(t^n) = nt^{n-1}$$

$$\frac{d}{dt}(e^{at}) = ae^{at}$$

$$\frac{d}{dt}(\sin \omega t) = \omega \cos \omega t$$

$$\frac{d}{dt}(\cos \omega t) = -\omega \sin \omega t$$

Integrals (omit +C):

$$\int t^n dt = \frac{t^{n+1}}{n+1}$$

$$\int e^{at} dt = \frac{1}{a} e^{at}$$

$$\int \sin \omega t dt = -\frac{1}{\omega} \cos \omega t$$

$$\int \cos \omega t dt = \frac{1}{\omega} \sin \omega t$$

PARTIAL FRACTION DECOMPOSITION

Used to invert complex $F(s)$ into time-domain components.

- **Distinct Real Roots:** $\frac{K}{(s-a)(s-b)} = \frac{A}{s-a} + \frac{B}{s-b}$

Heaviside Cover-up: $A = (s-a)F(s)|_{s=a}$

- **Repeated Roots:** $\frac{K}{(s-a)^2} = \frac{A}{(s-a)^2} + \frac{B}{s-a}$

- **Complex Roots:** Complete the square for the denominator: $s^2 + cs + d \Rightarrow (s-a)^2 + b^2$.

Expand as: $\frac{A(s-a)}{(s-a)^2 + b^2} + \frac{B(b)}{(s-a)^2 + b^2}$.

Inverse transforms directly to: $Ae^{at} \cos(bt) + Be^{at} \sin(bt)$.

CIRCUIT ANALYSIS & OP-AMPS

Transfer Functions ($H(s)$):

The ratio of the Laplace transform of the output to the input, assuming zero initial conditions: $H(s) = \frac{V_{out}(s)}{V_{in}(s)}$.

- **Poles & Zeros:** Roots of the numerator are **zeros** (frequencies where output is 0). Roots of the denominator are **poles** (these dictate system stability and the natural, transient response).

- **Frequency Response:** Substitute $s = j\omega$ into $H(s)$ to evaluate the system's magnitude $|H(j\omega)|$ (Gain) and phase shift $\angle H(j\omega)$ at specific frequencies.

- **Tip:** Treat capacitors and inductors as complex impedances (Z) and use standard DC analysis techniques (voltage dividers, node voltage) to solve for V_{out} in terms of V_{in} .

Standard Op-Amp Configurations (Ideal):

- Non-Inverting: $\frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_{in}}$

- Inverting: $\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$

Gain-Bandwidth Product (GBP):

- $GBP = A_v \times f_c$ (Gain $\times$ Cutoff Freq.)

- **Rule:** As single-stage gain increases, functional bandwidth decreases. Cascade stages to overcome this limitation.

STABILITY & NEGATIVE FEEDBACK

- **Frequency Domain Instability:** Identified by **Gain Peaking** (sharp spike in magnitude plot near cutoff frequency).

- **Time Domain Instability:** Identified by **Ringings** and **Overshoot** on a square wave step response.

- **Resolution:** Instability is caused by poles too close to the imaginary axis (low phase margin). Fix by adding a small **compensation capacitor** in parallel with the feedback resistor (adds a dominant pole).

DECOUPLING CAPACITORS

Real-world DC power lines contain noise. Capacitors are used to "clean" the signal.

- **Bulk Capacitors (e.g., 10 μ F electrolytic):** Filter low-frequency noise. Generally need 1 per board per power line. Can be placed anywhere on the rail.

- **Bypass Capacitors (e.g., 0.1 μ F ceramic):** Filter high-frequency noise. Must be placed *as close as possible* to the IC power pins. Need 1 per IC per power line.

LOADING EFFECT & IMPEDANCE

Ideal Component Impedances:

- Voltmeter / Oscilloscope: $Z_{in} = \infty$ (Open circuit)

- Ammeter: $Z_{in} = 0\Omega$ (Short circuit)

- Voltage Source: $Z_{out} = 0\Omega$

Loading Effect: Connecting a load forms a voltage divider: $V_{load} = V_{source} \left(\frac{Z_{in}}{Z_{out} + Z_{in}} \right)$.

- **Rule of Thumb:** To avoid voltage attenuation (signal loss), ensure $Z_{in} \gg Z_{out}$.

COMMON MODE REJECTION (CMRR)

Voltages & Gains:

- Differential Voltage (V_{DM}): $V_1 - V_2$

- Common Mode Voltage (V_{CM}): $\frac{V_1 + V_2}{2}$

- Output Voltage: $V_{out} = A_{DM}V_{DM} + A_{CM}V_{CM}$

CMRR Calculation:

- Ratio: $CMRR = \frac{A_{DM}}{A_{CM}}$

- Decibels (dB): $CMRR_{dB} = 20 \log_{10} \left(\frac{A_{DM}}{A_{CM}} \right)$

- **Concept:** High CMRR is desired to reject noise (like 60Hz wall interference) that appears simultaneously on both input lines.

EQUIPMENT & LAB PROCEDURES

Lab-Volt Power Supply:

- To provide $+V_{cc}$ and $-V_{cc}$, use a bridge connection: tie negative terminal of one supply to positive terminal of the other (creates COM).

- **Crucial:** Always set current limits to protect circuits from short-circuit damage!

Function Generator (50 Ω Load):

- Assumes it is driving a 50 Ω load.

- If circuit has high input impedance (e.g., op-amp), $V_{load} \approx V_{int}$. Output voltage will be roughly *double* the display unless using a 50 Ω terminating resistor.

Tektronix Oscilloscope:

- **Probe Comp (x10):** Calibrate using test square wave.

Overcompensated: Leading edge spike.

Undercompensated: Rounded leading edge.

Properly Compensated: Flat, crisp square wave.

- **Amplitude Scaling:** Scale waveform to fill vertical display without clipping to maximize ADC resolution.

ANALOG-TO-DIGITAL (ADC)

- **Signal Conditioning:** Shift and scale a small, bi-polar input signal to fit an ADC's input range. Apply a **DC offset** to center the signal, then **amplification** to stretch it.

- **SNR (Ideal):** For an N -bit ADC, $SNR_{dB} \approx 6.02N + 1.76$.

- **Nyquist Theorem:** Sampling rate must be at least twice the maximum frequency ($f_s \geq 2f_{max}$) to avoid aliasing.

EXAMPLE PROBLEMS & SETUP

1. Complex Numbers & Polar Conversion

Prob: Given $Z_1 = 3 + j4$, $Z_2 = 5\angle 30^\circ$, find $Z_1 \times Z_2$.

Sol:

1) Convert Z_1 : $r = \sqrt{3^2 + 4^2} = 5$.

2) Angle: $\theta = \tan^{-1}(4/3) \approx 53.13^\circ \Rightarrow Z_1 = 5\angle 53.13^\circ$.

3) Multiply magnitudes, add angles: $5 \times 5 = 25$, $53.13^\circ + 30^\circ = 83.13^\circ$.

Ans: $25\angle 83.13^\circ$

2. s-Domain to Time-Domain

Prob: $V_{out}(s) = \frac{10}{s+500}$, find $v_{out}(t)$.

Sol:

1) Standard Pair: $\mathcal{L}^{-1} \left\{ \frac{A}{s+a} \right\} = Ae^{-at}u(t)$.

2) Map variables: $A = 10$, $a = 500$.

Ans: $V_{out}(t) = 10e^{-500t}u(t)$ V

3. Complex Signals, Impedance, RMS

Prob: $v(t) = 10 \sin(1000t)$ V across a 0.1 μ F cap. Find V_{RMS} and Z_C .

Sol:

1) RMS Voltage: $V_{RMS} = \frac{V_{peak}}{\sqrt{2}} = \frac{10}{\sqrt{2}} \approx 7.07 V_{RMS}$.

- 2) Identify frequency: $\omega = 1000 \text{ rad/s}$.
 3) Impedance: $Z_C = \frac{1}{j\omega C} = \frac{1}{j(1000)(0.1 \times 10^{-6})} = \frac{1}{j(10^{-4})}$.
Ans: $-j10 \text{ k}\Omega$ (or $10 \angle -90^\circ \text{ k}\Omega$).

4. Active Circuit Transfer Function

Prob: Derive $H(s) = \frac{V_{out}}{V_{in}}$ for ideal non-inverting op-amp (R_f feedback, R_{in} to ground).
Sol:

- 1) Ideal rules: $V_+ = V_-$ and $I_{in} = 0$.
- 2) Find node voltages: $V_+ = V_{in} \Rightarrow V_- = V_{in}$.
- 3) KCL at V_- node: $\frac{V_- - 0}{R_{in}} + \frac{V_- - V_{out}}{R_f} = 0$.
- 4) Sub V_{in} : $V_{in} \left(\frac{1}{R_{in}} + \frac{1}{R_f} \right) = \frac{V_{out}}{R_f}$.

Ans: Multiply by R_f : $H(s) = 1 + \frac{R_f}{R_{in}}$.

5. Analog to Digital Converters

Prob: 10-bit ADC, 0V to 5V range. Find step size.
Sol:

- 1) Total discrete states: $2^n = 2^{10} = 1024$.
 - 2) Voltage Range: $V_{max} - V_{min} = 5V - 0V = 5V$.
 - 3) Step size: $\frac{\text{Range}}{\text{States}} = \frac{5V}{1024}$.
- Ans:** $\approx 4.88 \text{ mV}$.

6. Common Mode Rejection Ratio (CMRR)

Prob: An instrumentation amp has a differential gain $A_{DM} = 100$ and a common mode gain $A_{CM} = 0.01$. Find the CMRR in dB.
Sol:

- 1) CMRR Ratio: $\frac{A_{DM}}{A_{CM}} = \frac{100}{0.01} = 10000$.
 - 2) Convert to dB: $20 \log_{10}(10000) = 20(4)$.
- Ans:** 80 dB.

7. Coupled Op-Amps Transfer Function

Prob: Derive $H(s)$ for two cascaded op-amps (e.g., Stage 1: Inverting, Stage 2: Non-Inverting).
Foundational Setup:

- 1) Identify individual transfer functions: $H_1(s) = -\frac{R_{f1}}{R_{in1}}$ and $H_2(s) = 1 + \frac{R_{f2}}{R_{in2}}$.
- 2) Apply the cascade rule: $H_{total}(s) = H_1(s) \times H_2(s)$.
- 3) Self-Check: What happens to the overall phase if both stages are inverting?

8. Prelab 4, Problem 1 (LPF)

Prob: Find an expression for cutoff frequency f_c . Given $C_3 = 10 \mu F$, find f_c for $R_3 = [100\Omega, 1k\Omega, 10k\Omega, 100k\Omega]$.
Foundational Setup:

- 1) Foundation: First-order RC filter cutoff is $f_c = \frac{1}{2\pi RC}$.
- 2) Self-Check: Plug in the provided values. Remember μF is 10^{-6} !

9. Lecture 4a: ADC & Stability

Prob: Determine quantization step size and resolve ringing.
Foundational Setup:

- 1) Step size (ΔV) = $\frac{V_{range}}{2^N}$.
- 2) Stability Check: Ringing/peaking means poles are too close to the imaginary axis. Resolve by adding a parallel compensation capacitor to the feedback resistor.

10. HW 1: Problem 3b (Phasor Ops)

Prob: Given $f(t) = 12 \cos(200t + 45^\circ)$ and $g(t) = 5 \sin(200t + 102^\circ)$, find $h(t) = f(t) \cdot g(t)$.

Foundational Setup:

- 1) Convert sine to cosine: $\sin(\theta) = \cos(\theta - 90^\circ) \Rightarrow g(t) = 5 \cos(200t + 12^\circ)$.
- 2) Convert to phasors: $F = 12 \angle 45^\circ$, $G = 5 \angle 12^\circ$.
- 3) Multiply magnitudes, add phases, and convert back to time-domain.

11. HW 1: Problem 5 (Power Calculations)

Prob: Given $v(t) = 12 \cos(\omega t + 20^\circ)$ and $Z = -1.6971 + j1.6971 \Omega$. Find current $i(t)$, real power P , reactive power , and apparent power $|S|$.
Foundational Setup:

- 1) Convert Z to polar form: $r = \sqrt{x^2 + y^2}$, $\theta = \tan^{-1}(y/x)$. Hint: Watch your quadrant!
- 2) Phasor Current: $I = V/Z$. Remember to divide magnitudes and subtract angles. Convert the resulting phasor back to time-domain $i(t)$.
- 3) Apparent Power: $|S| = V_{RMS} I_{RMS} = \frac{1}{2} V_{peak} I_{peak}$.
- 4) Real / Reactive Power: $P = |S| \cos(\theta_z)$, $Q = |S| \sin(\theta_z)$, where θ_z is the angle of the impedance.

1.3b:

$$\begin{aligned} f(t) &= 12 \cos(200t + 45^\circ) \\ g(t) &= 5 \sin(200t + 102^\circ) \\ h(t) &= f(t) \cdot g(t) \\ \vec{F} &= 12 \angle 45^\circ = 12e^{j45^\circ} \\ &= 12[\cos(45^\circ) + j\sin(45^\circ)] \\ &= 12\cos(45^\circ) + j12\sin(45^\circ) \\ &= 8.4853 + j8.4853 \\ g(t) &= 5 \cos(200t + 102^\circ - 90^\circ) \\ &= 5 \cos(200t + 12^\circ) \\ &= 5 \angle 12^\circ \\ &= 5 \cos(12^\circ) + j5 \sin(12^\circ) \\ &= 4.8967 + j1.0396 \\ f(t) \cdot g(t) &\rightarrow \vec{F} * \vec{G} = (12 \cdot 5) \angle (45^\circ + 12^\circ) \\ &= 60 \angle 57^\circ \\ h(t) &= 60 \cos(200t + 57^\circ) \end{aligned}$$

1.5a:

$$\begin{aligned} v(t) &= 12 \cos(\omega t + 20^\circ) \\ Z &= -1.6971 + j1.6971 \\ \vec{V} &= 12 \angle 20^\circ \\ Z &= \sqrt{R^2 + X^2} \angle \tan^{-1}\left(\frac{X}{R}\right) \\ &= \sqrt{(-1.6971)^2 + (1.6971)^2} \angle \tan^{-1}\left(\frac{1.6971}{-1.6971}\right) [180^\circ] \\ &= 2.4 \angle 135^\circ \\ \vec{I} = \frac{\vec{V}}{Z} &= \frac{12}{2.4} \angle (20^\circ - 135^\circ) = 5 \angle -115^\circ \\ i(t) &= 5 \cos(\omega t - 115^\circ) \end{aligned}$$

LS 4a:

ADC # of bits: N
 # of levels = 2^N
 Input Voltage Range
 Q: How many volts does each level's step-size represent?
 $N=8$ & input voltage range = $[-1V, +1V]$
 $\text{Volts/level} = \frac{\text{voltage range}}{\# \text{ of levels}} = \frac{2V}{256 \text{ levels}} \approx 7.8 \text{ mV/level}$
 $2^8 = 256$ $2V$
 Q: What voltage is represented by 0000 0110?
 $= 6$
 $6 \text{ levels} * 7.8 \text{ mV/level} = 46.8 \text{ mV (from the bottom)}$
 $-1V + 0.0468V = -0.9532V$

PL 4.1 Derive the transfer fn.

$$\begin{aligned} H(j\omega) &= \frac{V_{out}}{V_{in}} \\ V_{out} &= V_{in}^* \\ V_- &= V_{out}^* \\ V_{out}^* &= \frac{R_1}{R_1 + R_2} V_s \\ &= \frac{R_1}{R_1 + R_2} V_{in}^* \\ V_{in} &= \frac{R_1 + R_2}{R_1} V_{out} \\ \frac{R_1 + R_2}{R_1} &= \frac{V_{out}}{V_{in}} \\ &= \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1} = H(j\omega) \end{aligned}$$

2.5, 2.6

$$\begin{aligned} R &= 560 \Omega & i(0) &= 0A \\ L &= 100 \text{ mH} & i'(0) &= 1000 \text{ A/s} \\ C &= 0.1 \mu F \\ I(s) &= \frac{i(0)s + [i'(0) + \frac{R}{L}i(0)]}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \\ &= \frac{-a \pm \sqrt{a^2 - 4b}}{2} = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{1}{LC}}}{2} \\ &= \frac{-2800 \pm j9600}{2} \\ s^2 + as + b &= (s + c)^2 + d \\ c = \frac{a}{2} = \frac{R}{2L} & \& d = b - \frac{a^2}{4} = \left[\frac{1}{LC} - \left(\frac{R}{2L}\right)^2\right] \\ \frac{i(0)s + [i'(0) + \frac{R}{L}i(0)]}{(s + \frac{R}{2L})^2 + [\frac{1}{LC} - (\frac{R}{2L})^2]} &= \frac{A}{s + \frac{R}{2L}} + \frac{B}{s + \frac{R}{2L} + j\sqrt{\frac{1}{LC} - (\frac{R}{2L})^2}} \\ i(0)s + [i'(0) + \frac{R}{L}i(0)]s &= A[s + \frac{R}{2L}] + B[s + \frac{R}{2L} + j\sqrt{\frac{1}{LC} - (\frac{R}{2L})^2}]s \\ i(0) &= A + D \\ i'(0) + \frac{R}{L}i(0) &= A(\frac{R}{2L}) + B[\frac{R}{2L} + j\sqrt{\frac{1}{LC} - (\frac{R}{2L})^2}] \\ i(0) &= 1000 = B(9600) & I(s) &= 0.1042 \left[\frac{9600}{(s + 2800)^2 + 9600^2} \right] \\ B &= \frac{1000}{9600} \approx 0.1042 & \text{Inverse Laplace Fcn (419 on slide)} & \\ i(t) &= 0.1042 e^{-2800t} \sin(9600t) A & t \geq 0 & \end{aligned}$$